

# DIGITAL INTELLECTUAL PROPERTY CORES (IP) DESIGN

Trinh Quang Kien Ph.D.

[kien.trinh@lqdtu.edu.vn# quangkien82@gmail.com](mailto:kien.trinh@lqdtu.edu.vn#quangkien82@gmail.com)




Course URL: <https://sites.google.com/view/trinhquangkien/Courses/>

# LECTURE 1.3 OUTLINE

- Introduction of FPGA
  - What is an FPGA?
  - FPGA architecture
  - FPGA configurability
  - FPGA resources
   
# WHAT IS THE FPGA?

- *FPGA\** (Xilinx.com):
  - **Field-programmable** Gate Arrays are semiconductor devices that are based around a matrix of configurable logic blocks (CLBs) connected via programmable interconnects. FPGAs can be **reprogrammed** to desired application or functionality requirements **after manufacturing**.
- *Other means to build a digital system:*
  - ASICs Application-Specific Integrated Circuits
  - ASSPs Application-Specific Standard Products



\* *Modern FPGA is an integrated IC based on CMOS technology*

# FPGA APPLICATIONS

## Implementation of random logic

- easier changes at system-level (one device is modified)
- can eliminate need for full-custom chips

## Prototyping

- ensemble of gate arrays used to emulate a circuit to be manufactured
- get more/better/faster debugging done than possible with simulation

## Reconfigurable hardware


- one hardware block used to implement more than one function
- functions must be mutually-exclusive in time
- can greatly reduce cost while enhancing flexibility
- RAM-based only option

## Special-purpose computation engines

- hardware dedicated to solving one problem (or class of problems)
- accelerators attached to general-purpose computers
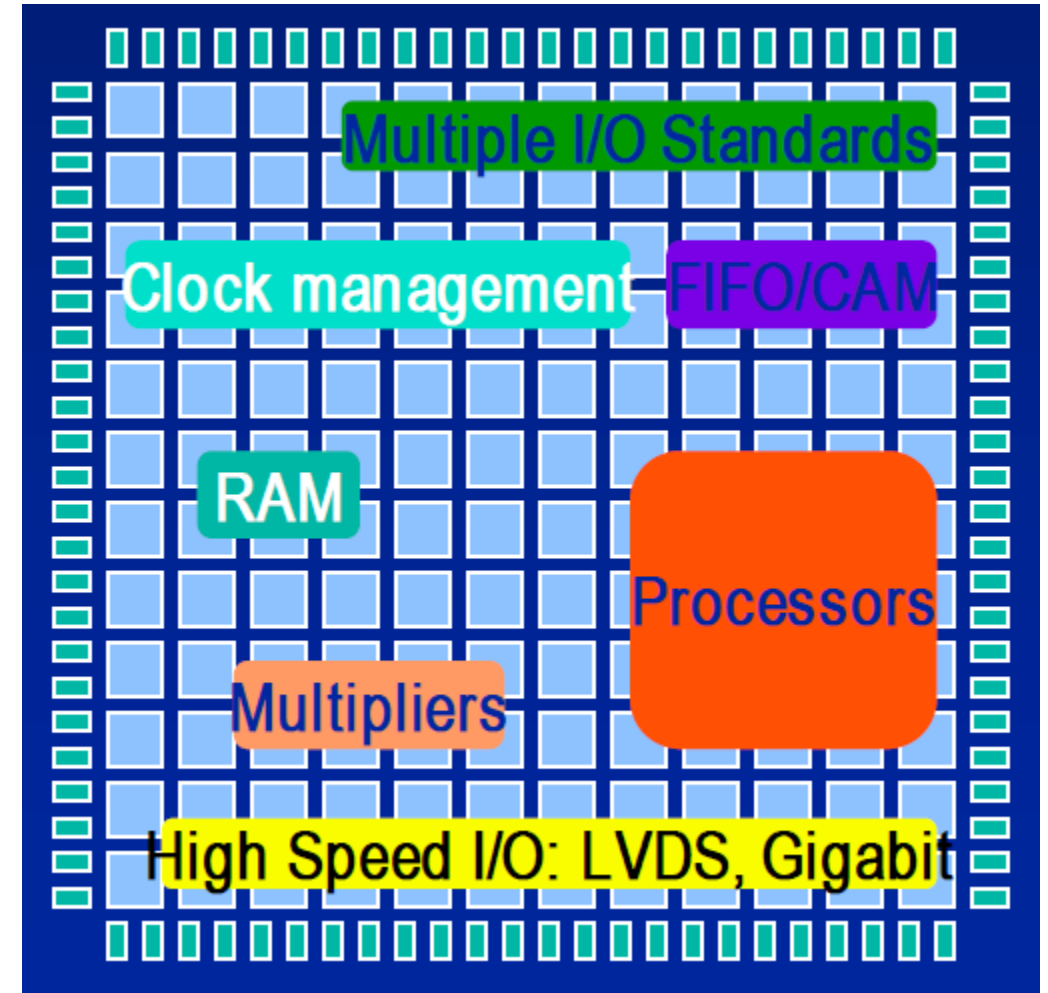
# FPGA ARCHITECTURE

- **configurable logic blocks** (up to 10 millions gates)
- **configurable interconnects**
- **configurable IO pads** (large number 100-1000 pins)
- Two-dimensional array (matrix) architecture: scalable
- state-of-the-art CMOS process (most advanced 7nm),
  - High speed (up to 500 Mhz logic core)
  - High density (tens of billion transistor count)
- Integrated dedicated IPs
  - DSP
  - Block RAM (SRAM-based)
  - Embedded CPU
  - High-speed IO (GTP (6.5Gbps), GTX (12Gbps), GTZ (32Gbps), 100Gbps Ethernet, 150Gbps Interlake)
  - AI engines (Versal FPGA)
- Low-cost reconfigurability by the end user




# IC INTEGRATION

IC	Transistor count	Process	Manufacture	Year
Intel 4004	2 300	10 um	Intel	1971
Zilog Z80	8 500	4 um	Zilog	1976
Intel 80286	164 000	1.5 um	Intel	1982
Pentium 2	7 500 000	0.35um	Intel	1997
Pentium 4	42 000 000	180 nm	Intel	2000
Core 2 Duo	291 000 000	65 nm	Intel	2006
Six core Xenon 7400	1 900 000 000	45 nm	Intel	2008
10-Core Xeon	2 600 000 000	32 nm	Intel	2010
GK110 Kepler	7,080,000,000	28nm	NVIDIA	2012
AMD K8	106 000 000	130 nm	AMD	2003
Spartan 3E	~40 000 000	90 nm	Xilinx	1998
Virtex 5	1 100 000 000	65 nm	Xilinx	2006
Starix IV	2 500 000 000	40 nm	Altera	2008
Starix V	3 800 000 000	28 nm	Altera	2011
Virtex 7	~6 800 000 000	28nm	Xilinx	2011
<u>Versal</u> VC1902	37,000,000,000	7nm	Xilinx	2H 2019


[https://en.wikipedia.org/wiki/Transistor\\_count](https://en.wikipedia.org/wiki/Transistor_count)
 
# FPGA PROGRAMMABILITY

- SRAM-based (volatile memory) configuration file (bitstream)
- Permanent configuration
  - Serial Peripheral interface (SPI) Flash
  - Byte-peripheral interface BPI Flash
- Others options (outdated FPGA)
  - Fused and anti-fused (one time)
  - EPROM and EEPROM (high power consumption, difficult for integration)





XAPP587\_10\_051512

 

# FPGA PROGRAMMABLE LOGIC

- Which universal circuit can do all logic functions?
- Logic function representation ?
  - Boolean function
  - Schematics
  - **Truth table**
- Two equivalent circuit?
  - *Which-ever input results in the same output*
- Classic theorem:
  - All logic functions can be implemented via basic gates


Any less than or equal to 2 input gates

 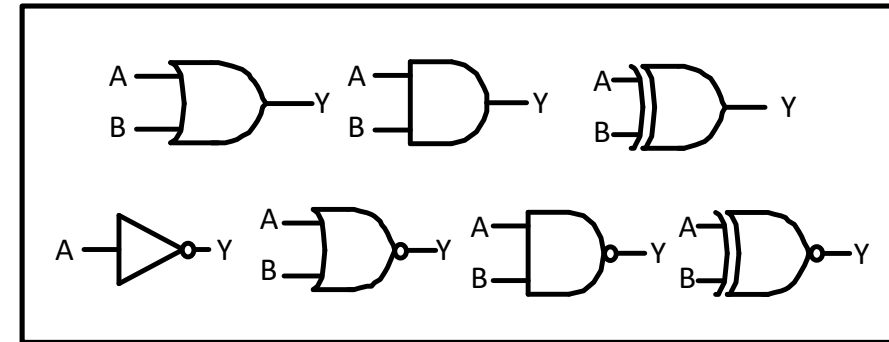




# FPGA PROGRAMMABLE LOGIC: EXAMPLE #1

- XOR gate equivalent 2-input LUT

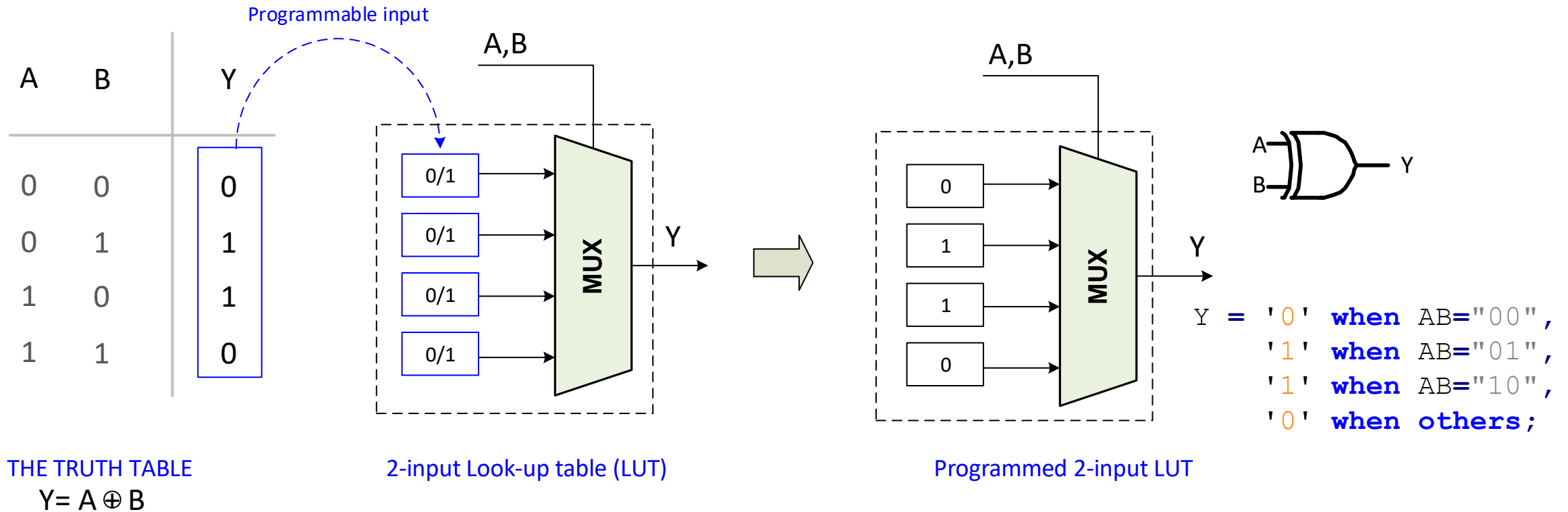


# FPGA PROGRAMMABLE LOGIC: EXAMPLE #2

- More complicated functions

 


# FPGA PROGRAMMABLE LOGIC: EXAMPLE #2

- More complicated functions

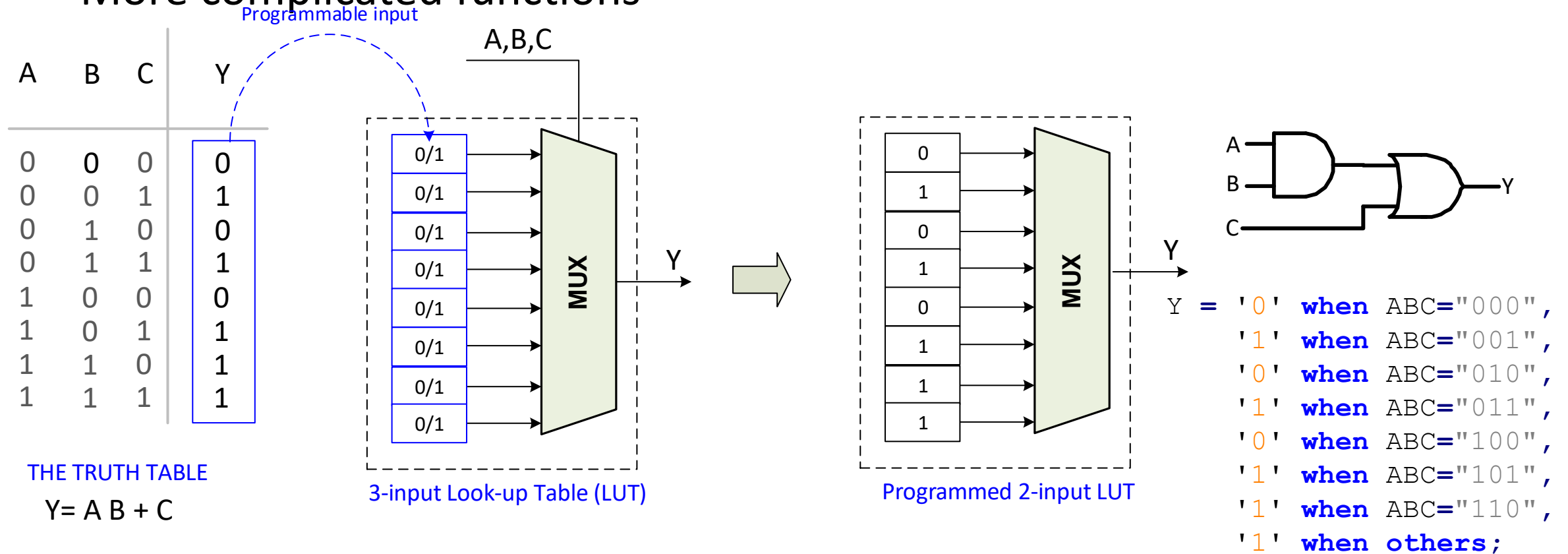


# FPGA PROGRAMMABLE LOGIC: LUT

- 4-LUT vs 6 LUT in FPGA

 

Spartan 3/3E 4 input LUT

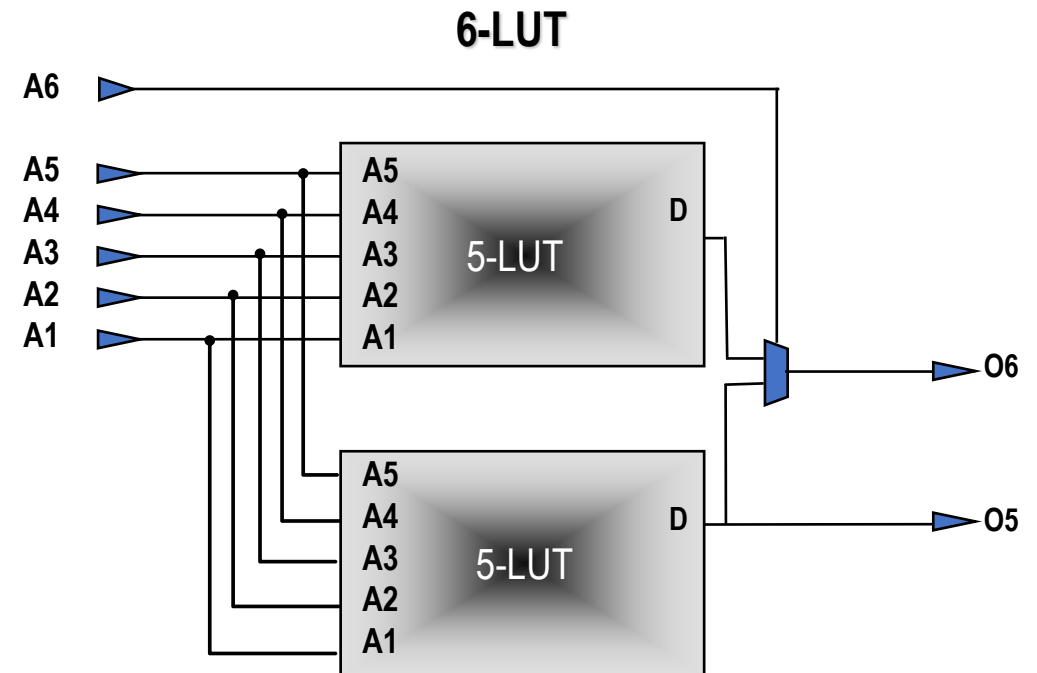


Series 7 6-input LUTs

# FPGA WIDE MULTIPLEXER

- How to implement larger number of input functions?



$$O_5 = F_{5(A_5, A_4, A_3, A_2, A_1)} = \begin{cases} F_5(0, A_4, A_3, A_2, A_1) & \text{when } A_5=0 \\ F_5(1, A_4, A_3, A_2, A_1) & \text{when } A_5=1 \end{cases}$$
 
$$= \begin{cases} F_{4,0}(A_4, A_3, A_2, A_1) & \text{when } A_5=0 \\ F_{4,1}(A_4, A_3, A_2, A_1) & \text{when } A_5=1 \end{cases}$$



 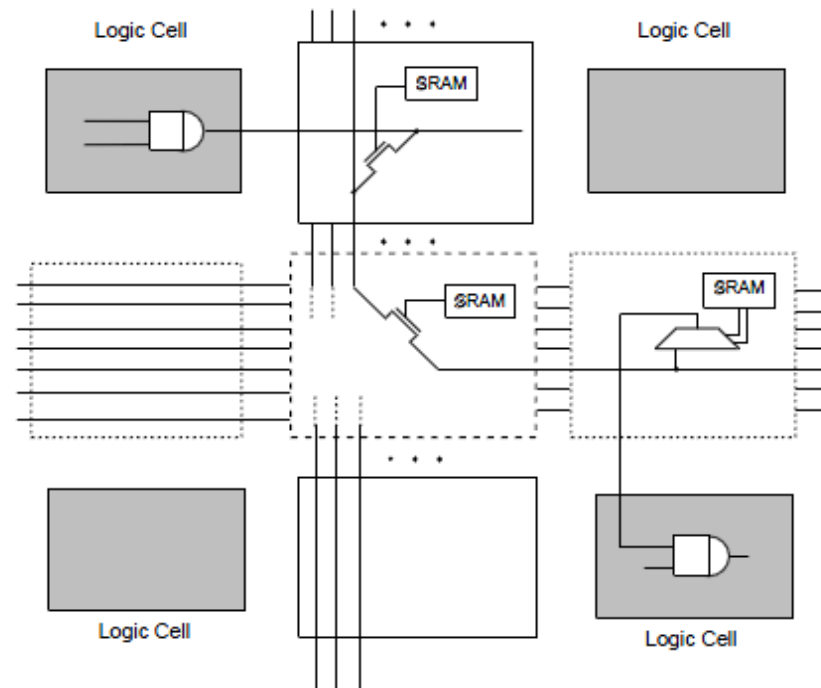
# FPGA PROGRAMMABLE INTERCONNECT

- Routing is done by a pass transistor (switch)
  - 1: connected
  - 0: isolated
- Routing lines
  - Direct
  - Double/single
  - Long line
  - Global


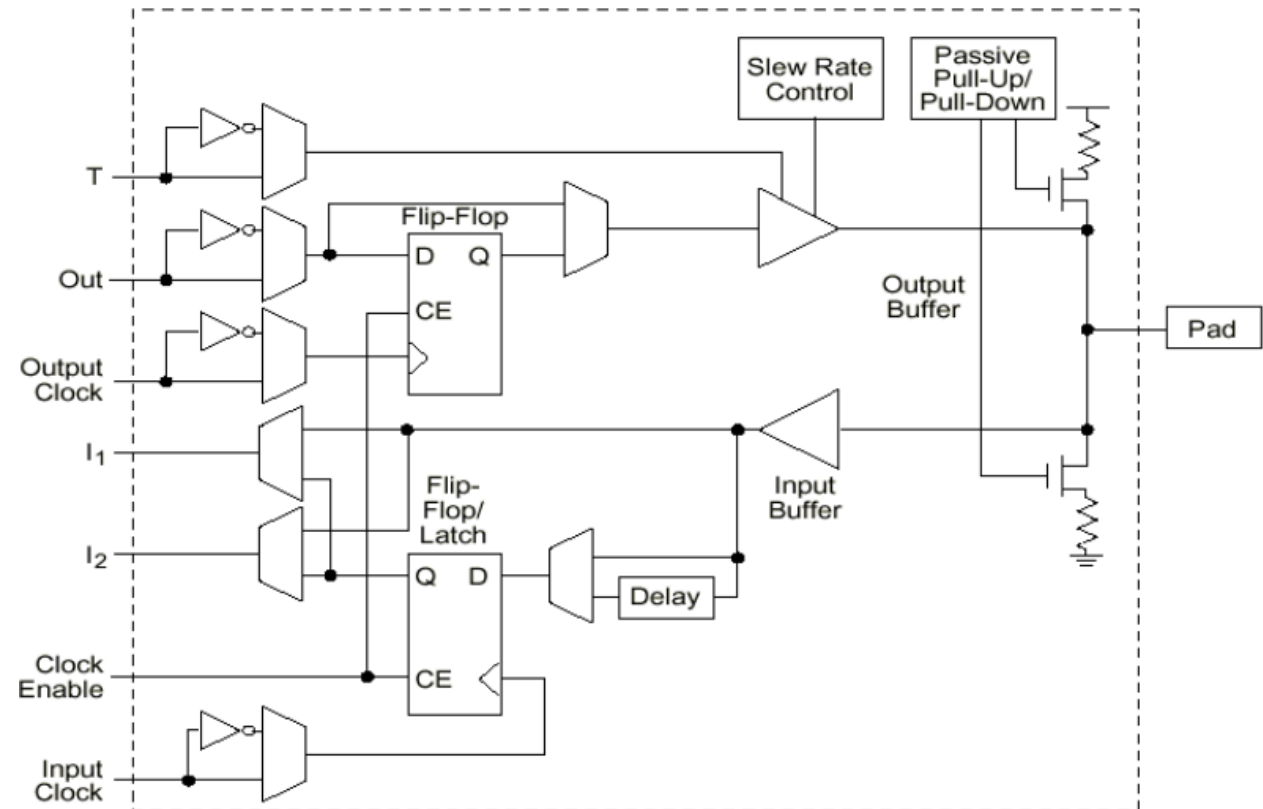
# FPGA PROGRAMMABLE IO

- Majority IO are inout Pin
- Signal can be delayed by a programmable value
- Support double data rate (DDR)
- Programmable voltage
- GTP, GTX, GTX for Gigabit serial transmission (all are LVDS)



# FPGA FURTHER READING TOPIC

- Examples of FPGA Architectures
  - [Spartan 3 Architectures](#)
  - [Spartan-6 FPGA Configurable Logic Block](#)
  - [7 Series FPGAs Configurable Logic Block](#)
- [FPGA for dummies](#) 😊

